



## HOMEWORK #1

### CS 303 – Digital Design

Date: 17/10/2019

Due Date: 24/10/2019

#### 1. Number systems

- Convert the decimal number 44 into: binary, octal, hexadecimal
- Convert the unsigned binary number 10100111.110 into: decimal, octal, hexadecimal
- Convert the octal number 177 into: binary, decimal, hexadecimal
- Find the base X if the following is true:  $123_{(X)}=63_{(15)}$

#### 2. Only in CS303 - Aliens come....


- You meet an alien! He waves you with his four hands... and gives you 32 apples as a sign of his friendship. However, he says he gave you 20, not 32 apples!!! (But you are both right.) How many fingers does he have on each hand?
- He says he will be back in 100 (Earth) years! What (Earth) year will that be? It is 2019 now...

#### 3. Negative binary numbers, addition and subtraction

- Express  $(-55)_{10}$  in binary format using two's complement method.
- Perform subtraction using 2's complement of the subtrahend:
  - $01111001 - 00110101$
  - $11101101 - 01111011$
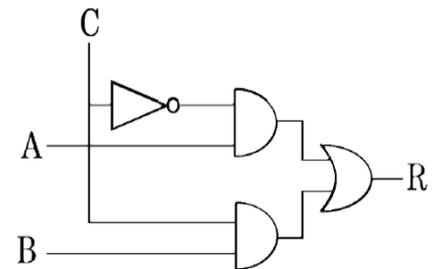
#### 4. Logic gates

- Obtain an expression for R from the diagram on the right:
- Make the truth table of the circuit!
- Give the truth table in form of a Karnaugh map and check whether the circuit is optimized!
- Sketch an alternative circuit that implements the same function as POS.



#### 5. Simplify the following Boolean functions to a minimum number of literals:

- $(x + y)(x + y')$
- $xyz + x'y + xyz'$
- $(x + y)'(x' + y')$

#### 6. There are three bits A, B and C that form a number from 0 to 7 (000=0, 001=1, 010=2, 011=3...). Design function F(A,B,C) that is logical "1" when the number is divisible by 3 without a remainder, otherwise "0".

- Make the truth table of the function F. Obtain the expression for the output F, first as a **sum of minterms**, and then as a **product of maxterms**!
- Try then to reduce the expression for F by using Karnaugh map!
- Show the result as POS and SOP! Finally, show that  $SOP = POS$  by Boolean algebra manipulation!